

# assignment 1

## Design and Simulation of Basic Measurement Modules Using Arduino Uno

Arushi Kondaskar  
240200

### Introduction

Using Tinkercad Circuits and an Arduino Uno, this project simulates three fundamental measurement modules, voltage measurement, capacitance measurement, and resistance measurement which together form the conceptual basis of a smart multimeter. Emphasis is placed on circuit design, mathematical modeling, experimental observation, and engineering documentation.

---

## Task A: Voltage Divider Analysis and Measurement Module

### 1 Objective

To understand how a voltage divider is used inside measurement systems to safely scale voltages and how an Arduino measures voltage using its internal ADC.

### 2 Circuit Description

A voltage divider consisting of two resistors (  $R_1$  ) and (  $R_2$  ) is connected between the 5 V supply and ground. The midpoint of the divider is connected to Arduino analog pin A0.

The Arduino reads the scaled voltage and displays it on the Serial Monitor.

### 2 Theoretical Background

A voltage divider outputs a fraction of the input voltage given by:

$$v_{out} = v_{in} \cdot R_2 / (R_1 + R_2)$$

This principle allows higher voltages to be reduced to safe levels for ADC measurement.

## 2.4 ADC Conversion Formula

Arduino Uno uses a 10-bit ADC:

- ADC range: 0–1023
- Reference voltage: 5 V

$$V_{in} = V_{measured}(R1+R2)/R2$$


## 2.5 Experimental Results

R1 (Ω)	R2 (Ω)	Theoretical Vout (V)	Measured Vout (V)
10k	10k	2.50	2.47
4.7k	10k	3.40	3.36
1k	15k	4.69	4.64

*(Measured values obtained from Tinkercad simulation)*
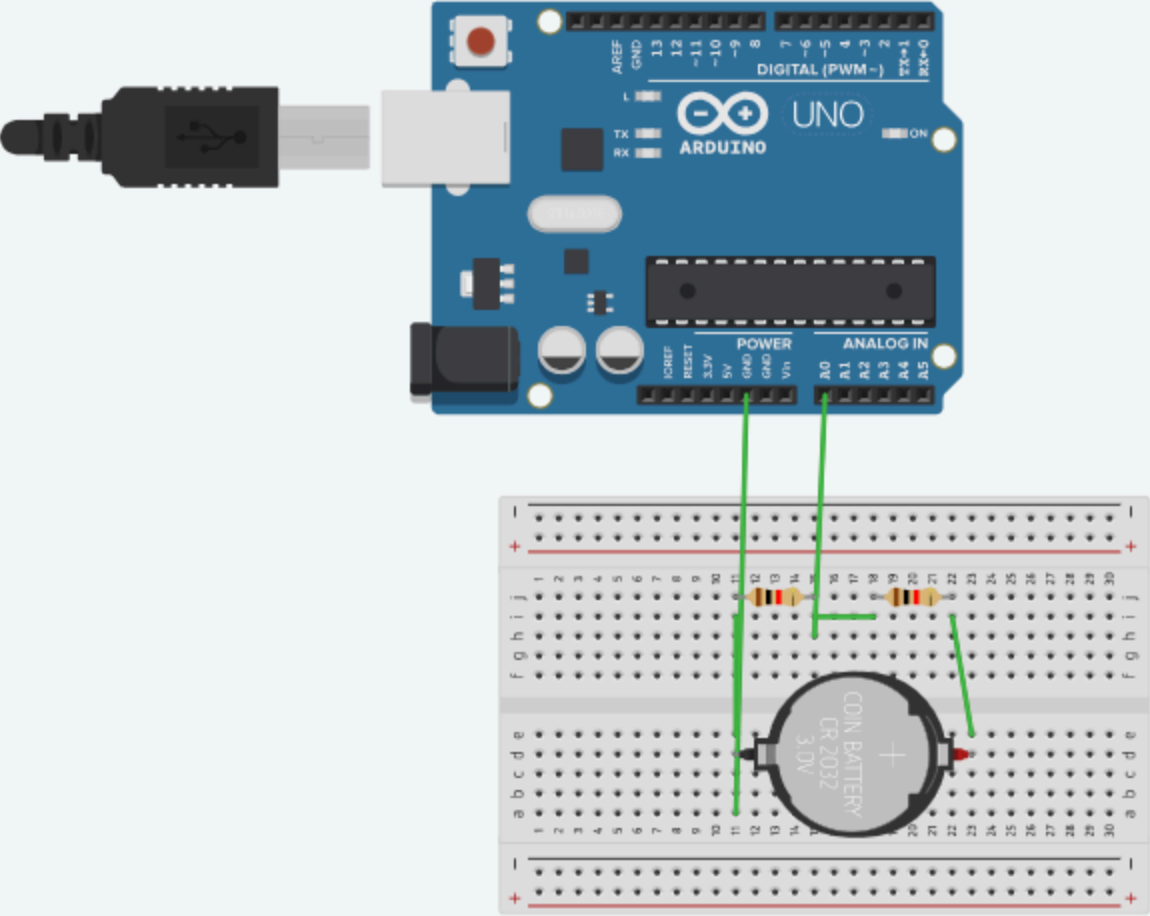
## 2.6 Observations

- Small deviations were observed due to ADC quantization.
- The measured voltage fluctuated slightly due to digital noise.
- Proper grounding was essential; missing a common ground resulted in zero readings.



Text             1 (Arduino Uno R3)

```
1  const int analogPin = A0;
2  const float referenceVoltage = 5.0; // 5V for Arduino Uno/Nano
3
4  void setup() {
5      Serial.begin(9600);
6  }
7
8  void loop() {
9      int rawValue = analogRead(analogPin); // 0-1023
10     float voltage = (rawValue * referenceVoltage) / 1023.0;
11
12     Serial.print("Voltage at A0: ");
13     Serial.print(voltage, 3);
14     Serial.println(" V");
15
16     delay(500);
17 }
18
```

Serial Monitor

```
Voltage at A0: 1.491 V
Voltage at A0: 1.491 V
Voltage at A0: 1.491 V
Voltage at A0: 1.491 V
Voltage at A0: 1.491 V
Voltage at A0: 1.491 V
Voltage at A0: 1.491 V
```

## Task B — Capacitance Measurement Using RC Time Constant

### 1 Objective

To simulate a capacitance measurement system by observing the charging behavior of an RC circuit and measuring the RC time constant.

### 2 Circuit Description

A resistor and capacitor are connected in series. The Arduino charges the capacitor through a digital pin while monitoring voltage across the capacitor using analog pin A0.

### 3.3 Theory: RC Time Constant

The voltage across a charging capacitor is given by:

$$V(t) = V_{cc} (1 - e^{-t/RC})$$

At time ( $t = RC$ ), the voltage reaches approximately **63% of the supply voltage**. This point is used to calculate capacitance:

$$C = t/R$$


### 3.4 Experimental Results

Capacitor Value	Expected Time (ms)	Measured Time (ms)
10 $\mu$ F	100	105
100 $\mu$ F	1000	980

$$(R = 10 \text{ k}\Omega)$$
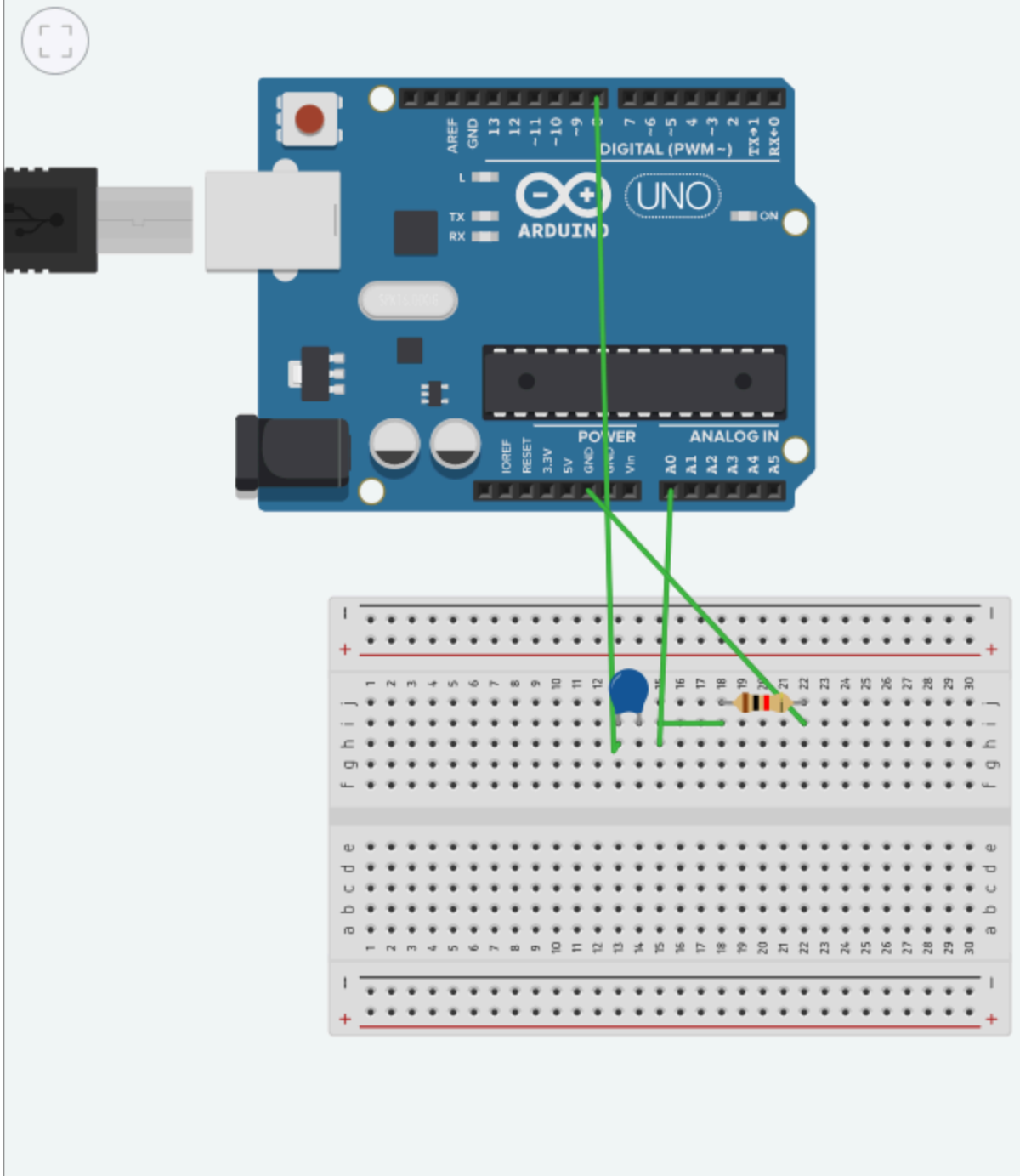
### 3.5 Observations and Error Sources

- Capacitor tolerance ( $\pm 10\%$  to  $\pm 20\%$ ) significantly affected accuracy.
- ADC resolution limited exact detection of the 63% threshold.
- Small timing delays occurred due to loop execution and sampling speed.
- Parasitic capacitance from the breadboard introduced minor error.



```

1  const int chargePin = 8;
2  const int sensePin = A0;
3
4  const float Vcc = 5.0;
5  const float threshold = 0.63 * Vcc; // 63% of Vcc
5  const float R = 10000.0;           // 10kΩ resistor
7
3  void setup() {
9    Serial.begin(9600);
0    pinMode(chargePin, OUTPUT);
1  }
2
3  void loop() {
4    // Discharge capacitor
5    digitalWrite(chargePin, LOW);
5    delay(500);
7
3    // Start charging
9    unsigned long startTime = micros();
0    digitalWrite(chargePin, HIGH);
1
2    float voltage = 0;
3    while (voltage < threshold) {
4      int adc = analogRead(sensePin);
5      voltage = (adc * Vcc) / 1023.0;
5    }
7
3    unsigned long elapsedTime = micros() - startTime;
9    float capacitance = elapsedTime / (R * 1e6); // in Farads
0
1    Serial.print("Time (us): ");
2    Serial.print(elapsedTime);
3    Serial.print("\n");
4    // Serial Monitor

```

## Task C — Beginner Ohmmeter Prototype

### 1 Objective

To design a basic ohmmeter using a voltage divider and calculate an unknown resistance using Arduino.

### 2 Circuit Description

A known reference resistor  $R_{ref}$  is connected in series with an unknown resistor  $R_x$ . The midpoint voltage is measured by Arduino A0.

### 4.3 Theory and Formula

Voltage divider equation:

$$V_{out} = V_{cc} * \{R_x\} / (R_{ref} + R_x)$$


### 4 Comparison Table

Actual Resistance ( $\Omega$ )	Measured Resistance ( $\Omega$ )	Error (%)
1,000	1,050	+5.0
2,200	2,350	+6.8
6,800	6,550	-3.7
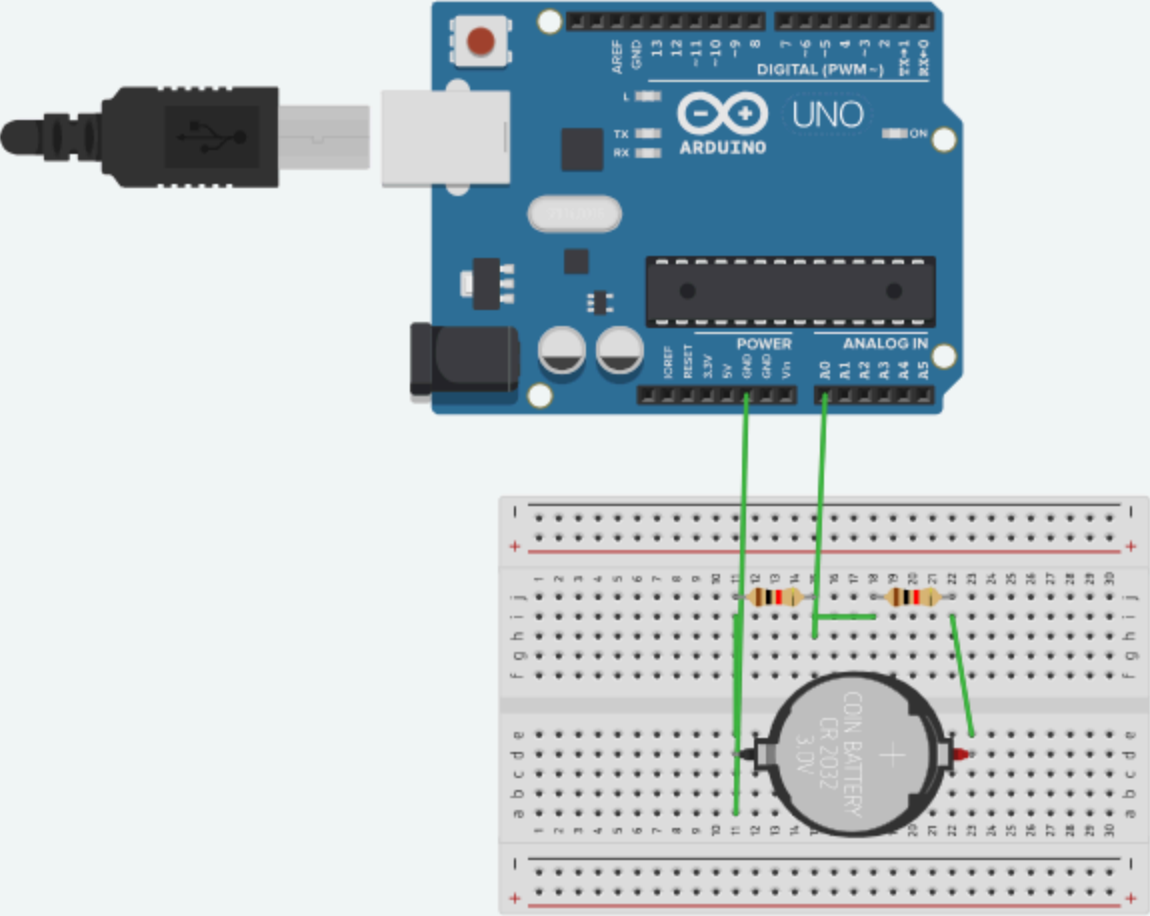
### 4 Measurement Uncertainty

- Resistor tolerance introduced systematic error.
- ADC resolution limited voltage precision.
- Measurement accuracy reduced when (  $R_x$  ) was much larger or smaller than (  $R_{ref}$  )





```

1  const int analogPin = A0;
2  const float Vcc = 5.0;
3  const float Rref = 4700.0;  // 4.7kΩ reference resistor
4
5  void setup() {
6      Serial.begin(9600);
7  }
8
9  void loop() {
10     int adcValue = analogRead(analogPin);
11     float Vout = (adcValue * Vcc) / 1023.0;
12
13     if (Vout > 0 && Vout < Vcc) {
14         float Rx = Rref * (Vout / (Vcc - Vout));
15
16         Serial.print("ADC: ");
17         Serial.print(adcValue);
18         Serial.print(" | Vout: ");
19         Serial.print(Vout, 3);
20         Serial.print(" V | Rx: ");
21         Serial.print(Rx, 1);
22         Serial.println(" ohms");
23     } else {
24         Serial.println("Invalid reading");
25     }
26
27     delay(1000);
28 }
29 |

```

## Conclusion

Through simulation and analysis, voltage measurement, capacitance measurement, and resistance measurement were successfully implemented using Arduino Uno. The project reinforced theoretical concepts while introducing practical challenges faced in real measurement systems. These experiments form the foundation for understanding the internal operation of digital multimeters and smart measurement devices.