

**Project Title:** Smart Multimeter Using Microcontroller System

**Assignment:**1

**Student Name:** Vanshika Khandelwal

**Roll Number:**241141

**Department:**EE


**Date:**14/12/25

## **#Introduction:**

This project seeks to build a simple monitoring system with an Arduino that helps grasp at the principles under which digital instruments measure electrical values. Experiment Goals: The goal of this experiment is to use basic theory of voltage dividers, RC time constants, and Ohm's laws to simulate measurements of several voltages, capacitance, and resistance.

Wiring Practical circuits are developed to transform analog electric signals into digital values using Tinkercad and the Arduino's ADC. These experiments illustrate the basic functionality of a common digital multimeter and show physical phenomena including ADC resolution, component variation, and measurement error.

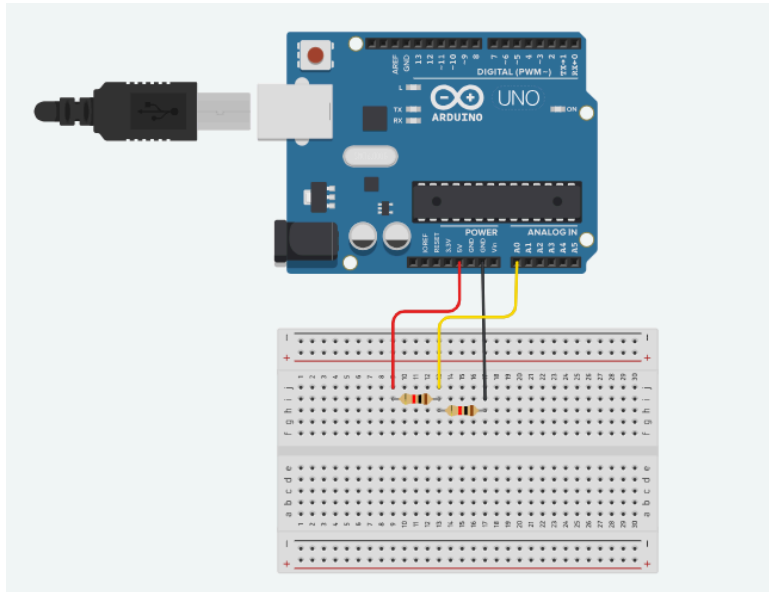
## # Task A — Voltage Divider Analysis and Measurement Module:




Text

```
1 // C++ code
2 //
3 void setup()
4 {
5     Serial.begin(9600);
6 }
7
8 void loop()
9 {
10    int adc=analogRead(A0);
11    float voltage=adc*(5.0/1023.0);
12    Serial.print("Voltage: ");
13    Serial.println(voltage);
14    delay(1000);
15 }
```


For  $R_1=R_2=10\text{ k}\Omega$

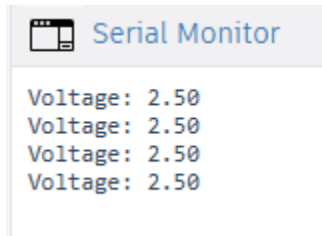

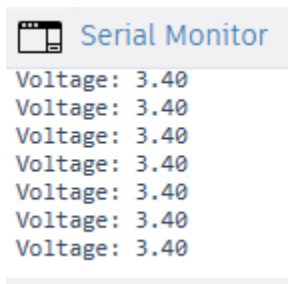For  $R_1=4.7\text{ k}\Omega$  &  $R_2=10\text{ k}\Omega$



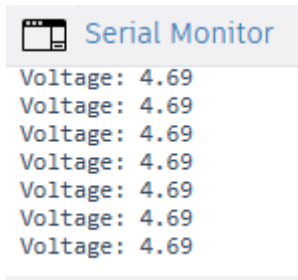For  $R_1=1\text{ k}\Omega$  &  $R_2=15\text{ k}\Omega$



-ADC to Voltage Conversion Formula:(10 bits)


$$V = \text{ADC} * (5/1023)$$

- Voltage Divider Formula:


$$V_{\text{out}} = V_{\text{in}} * [R_2 / (R_1 + R_2)]$$

Resistance values	Theoretical	Tinkercad Measured
R1=10k $\Omega$ R2=10k $\Omega$	2.5 V	2.5 V
R1=4.7k $\Omega$ R2=10k $\Omega$	3.4013 V	3.4 V
R1=1k $\Omega$ R2=15k $\Omega$	4.6875 V	4.69 V

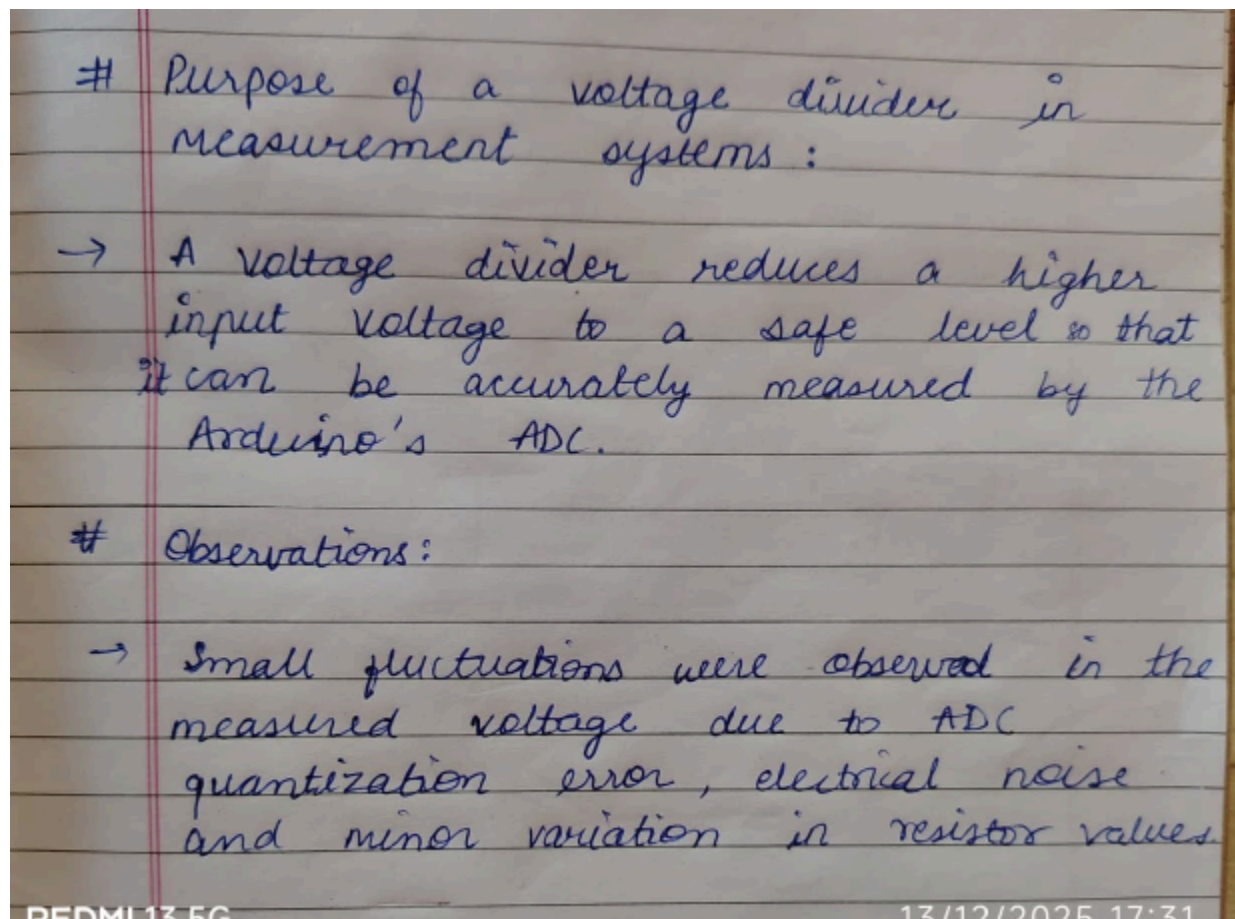Measured output voltages closely match the theoretical values calculated using the voltage-divider formula. Small deviations are observed due to the Arduino's 10-bit ADC resolution, electrical noise, and resistor tolerances etc.


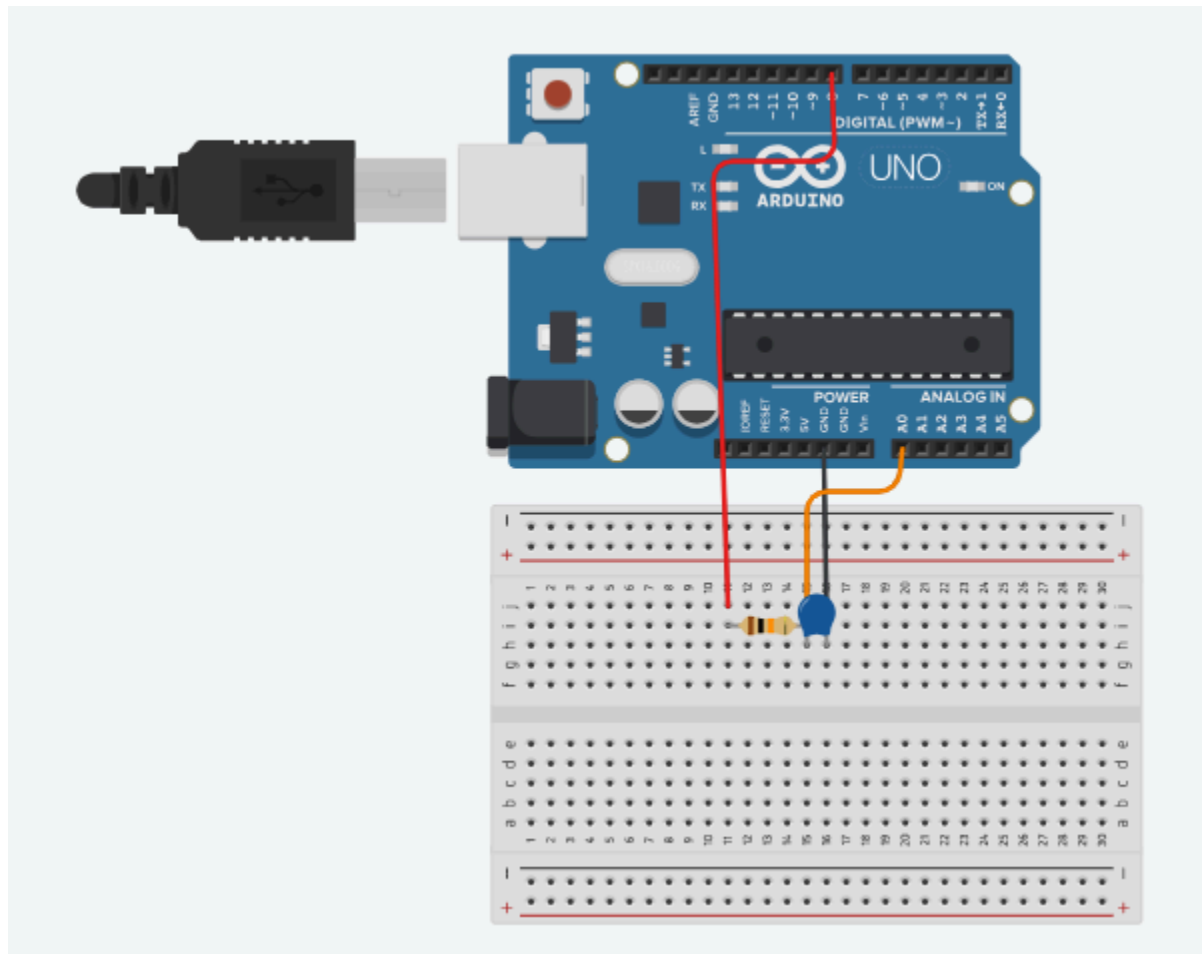
## **# Task 2— Capacitance Measurement Using RC Time Constant:**



```

1  const int chargePin=8;
2  const int analogPin=A0;
3  const float R=10000.0;
4
5  void setup(){
6      Serial.begin(9600);
7      pinMode(chargePin,OUTPUT);
8
9      digitalWrite(chargePin,LOW);
10     delay(2000);
11
12     digitalWrite(chargePin,HIGH);
13     unsigned long startTime = millis();
14
15     while(analogRead(A0)<0.63*1023){
16         // wait
17     }
18
19     unsigned long elapsed=millis()-startTime;
20     float C=elapsed/R;    // in millisecond/ohm
21     Serial.print("Time(ms): ");
22     Serial.println(elapsed);
23     Serial.print("Capacitance (approx): ");
24     Serial.println(C);
25 }
26
27 void loop() {}
28
29

```

For  $C=10\ \mu\text{F} = 0.01\ \text{ms}/\Omega$



Serial Monitor

Time(ms): 101

Capacitance (approx): 0.01

For  $C=100\ \mu\text{F} = 0.1\ \text{ms}/\Omega$



Serial Monitor

Time(ms): 1000

Capacitance (approx): 0.10

Capacitance Value	Measured Time	Expected Time(RC)
10 $\mu\text{F}$	101 ms	100 ms
100 $\mu\text{F}$	1000 ms	1000 ms


- ① The RC time constant ( $\tau = RC$ ) is the time required for a capacitor to charge to approx 63% of the supply voltage. This comes from the exponential charging law.

$$V_c(t) = V(1 - e^{-\frac{t}{RC}})$$

- ② Error Source:  
Error arise due to resistor & capacitor tolerance, electrical noise, ADC resolution & time limitations of millis().


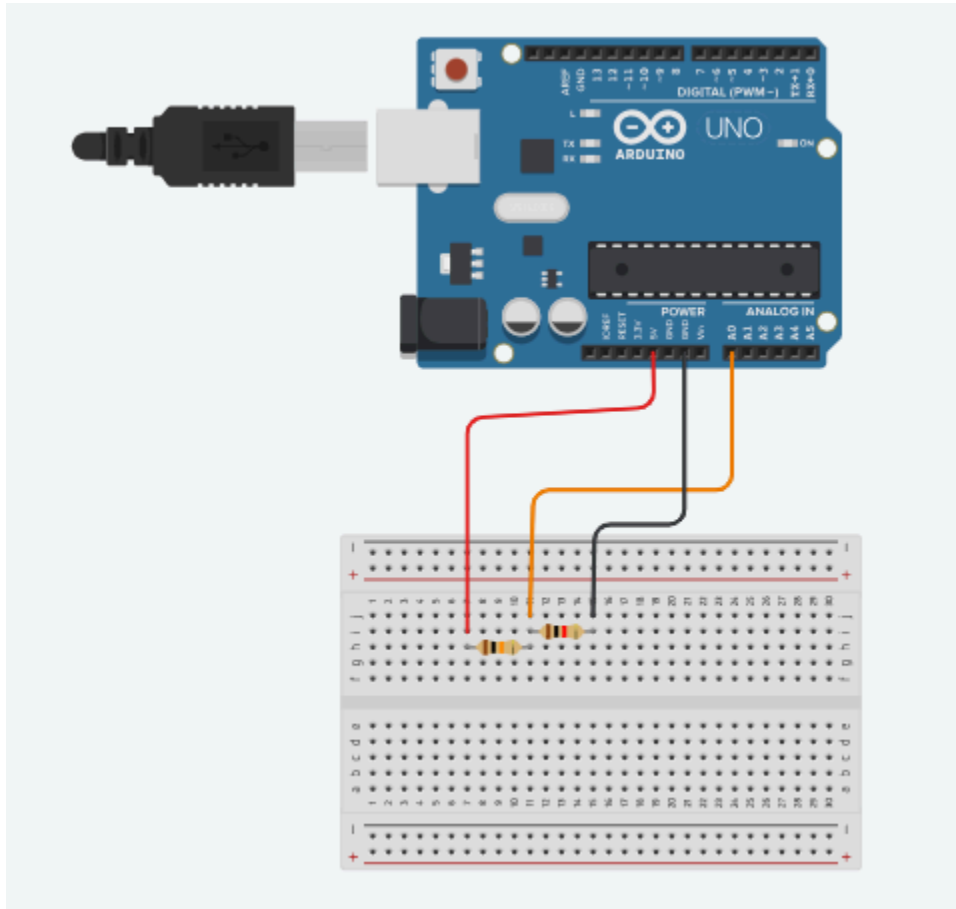
## **#Task C — Beginner Ohmmeter Prototype:**





For  $R_1=10\text{k}\Omega$ ,  $R_x=\text{Unknown}$ :



#### Serial Monitor

Measured Resistance (ohm): 4208.33  
Measured Resistance (ohm): 4208.33  
Measured Resistance (ohm): 4208.33  
Measured Resistance (ohm): 4208.33  
Measured Resistance (ohm): 4208.33  
Measured Resistance (ohm): 4208.33  
Measured Resistance (ohm): 4208.33

Known $R_1$	Unknown $R_x$ (Actual)	Unknown $R_x$ (Measured)
$10\text{k}\Omega$	$1\text{k}\Omega$	$1\text{k}\Omega$
$10\text{k}\Omega$	$11\text{k}\Omega$	$11.00616\text{ k}\Omega$
$10\text{k}\Omega$	$4.2\text{k}\Omega$	$4.20833\text{ k}\Omega$

① Step-by-step calculation:

The Arduino first converts the ADC reading into voltage using ADC formula.

ADC to Voltage conversion formula =

$$V_{out} = \text{ADC} \times \left( \frac{5}{1023} \right)$$

The unknown resistance is then calculated by rearranging the voltage divider eq.

$$V_{out} = V_{in} \left( \frac{R_x}{R_1 + R_x} \right)$$
$$R_x = R_1 \times \left( \frac{V_{out}}{V_{in} - V_{out}} \right)$$

② Measurement Uncertainty:

Small errors occur due to resistor tolerance, ADC resolution, electrical noise & reference voltage variation.

