

ASSIGNMENT 1

SMART MULTIMETER USING MICROCONTROLLER SYSTEMS

BY ISHWIN KUMAR
BTECH(ELECTRICAL
ENGINEERING)
ROLL NO: 240476



INTRODUCTION


Through this assignment, we use Arduino to find resistance, capacitance and voltages in simple RC circuits. Through a series of tasks, we determined capacitance and resistance using simple voltage divider and time constant equations.

Main objectives of this assignment are-

- 1) To verify the voltage divider rule experimentally using different resistor combinations.
- 2) To understand Arduino's Analog-to-Digital Converter.
- 3) To determine time constant of an RC circuit.
- 4) To calculate unknown resistance using voltage divider.


(TASK A)

1) 10kΩ–10kΩ:

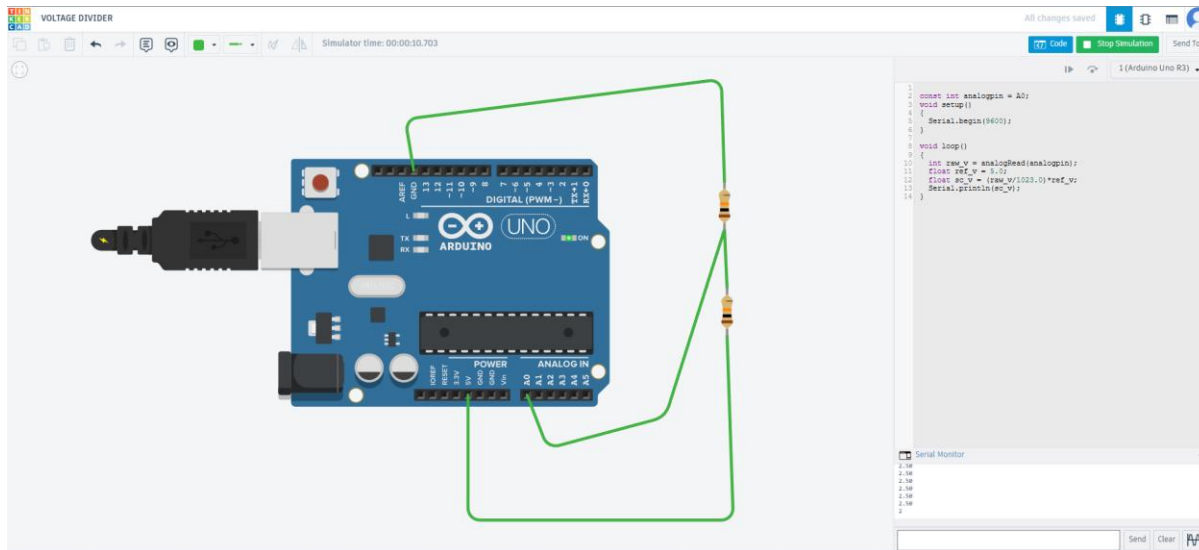

Experimental voltage measurer	Theoretical voltage measurer = $V_{in} \times (R_2 / (R_1 + R_2))$
2.5V	2.5V


2) 10kΩ–4.7kΩ:

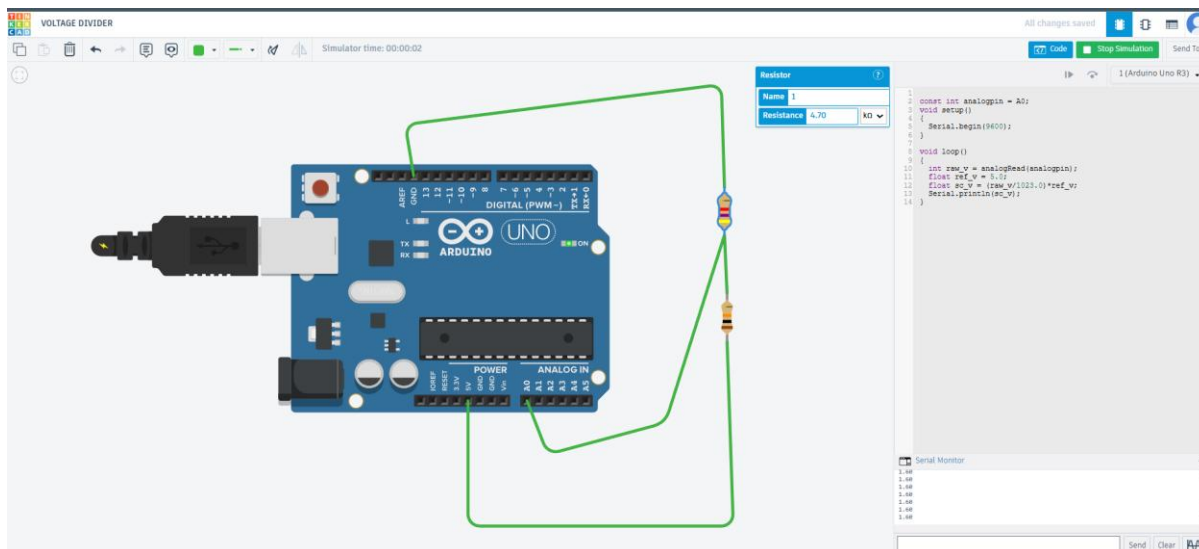

Experimental voltage measurer	Theoretical voltage measurer = $V_{in} \times (R_2 / (R_1 + R_2))$
1.60 V	$= 5.0 (4.7/14.7) = 1.598 \text{ V}$

3) 1kΩ–15kΩ:

Experimental voltage measurer	Theoretical voltage measurer = $V_{in} \times (R2 / (R1 + R2))$
0.31 V	= $5.0 (1/16) = 0.3125 V$

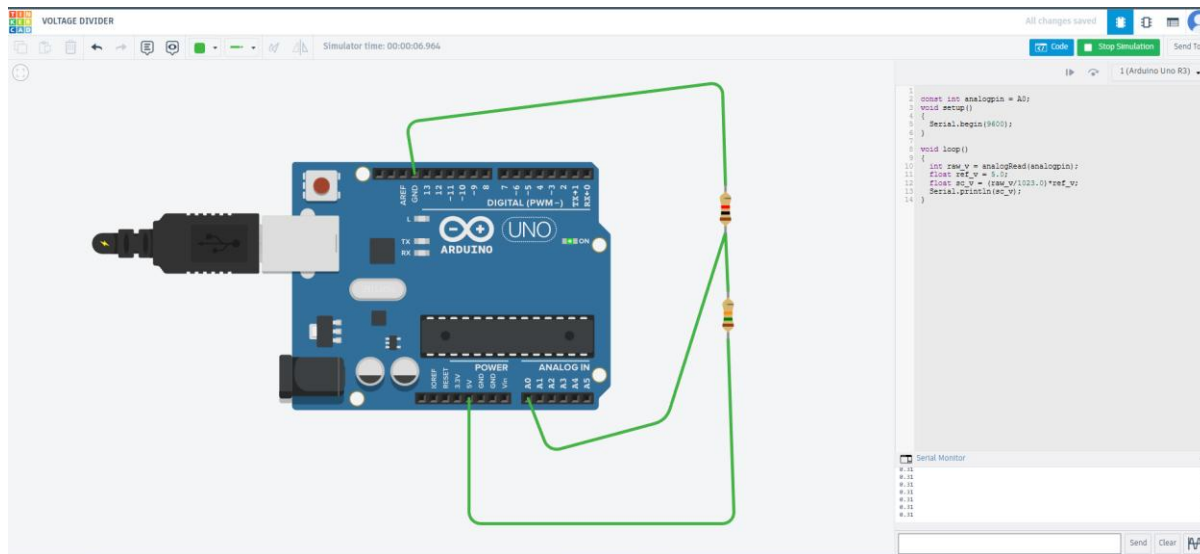

Arduino uses a 10-bit ADC, having ADC range: 0–1023 but we need Voltage range: 0–5V

Conversion Formula-

$$Voltage = ADC_value \times \frac{5.0}{1023.0}$$

Measurement Error

- Minor differences between theoretical and measured values occur due to:
- ADC resolution limits (± 1 –2 counts)

(TASK B)

$$V(t) = V_{cc}(1 - e^{-t/RC})$$


At $t = RC$


$$V(t) = 0.63 \times V_{cc}$$

Why 63% Is Significant

- At one time constant $\tau = RC$, the capacitor reaches 63% of its final voltage
- This gives a **direct and simple way** to calculate capacitance:

$$C = \frac{t}{R}$$

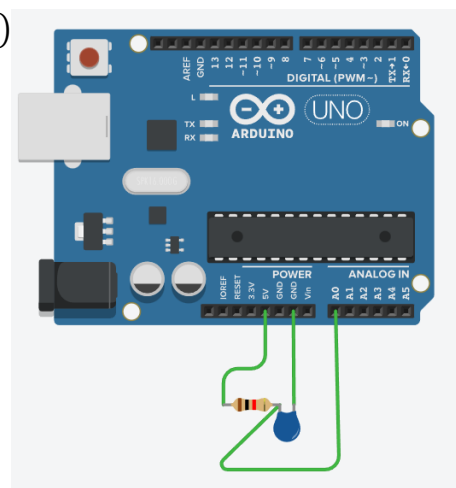

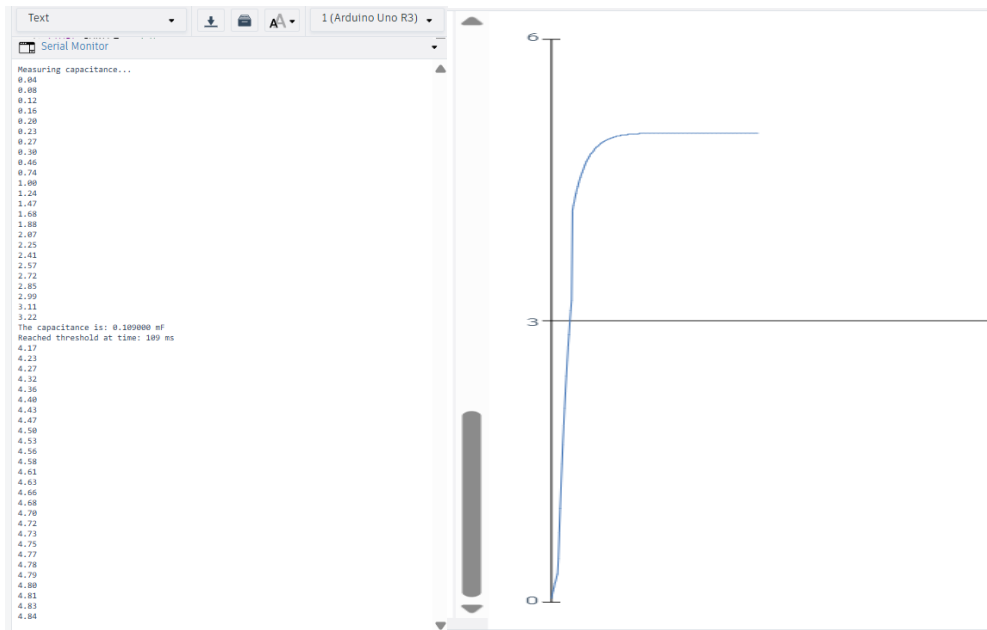

OUTPUT:

The output presents the voltage of capacitor in its charging phase at each milli second (the least count of Arduino time). Just as the voltage across capacitor crosses 63% of the Arduino provided input voltage, the elapsed time which is nothing but the time constant is shown on the screen. Using that, the capacitance is calculated.

CODE:

```
1  const int analo = A0;
2  float source = 5.0;
3
4  unsigned long starttime = 0;
5  bool measuring = false;
6  unsigned long time_elapsed;
7
8  float R = 1000.0; // 1k resistor
9
10 void setup() {
11   Serial.begin(9600);
12
13   measuring = true;
14   starttime = millis();
15
16   Serial.println("Measuring capacitance...");
17 }
18
19 void loop() {
20
21   int raw = analogRead(analo);
22   float A0_v = (raw / 1023.0) * source;
23
24   Serial.println(A0_v); // show the voltage rising
25
26   float threshold = 0.63 * source; // 63% of 5V = 3.15 V
27
28   if (measuring && A0_v >= threshold) {
29
30     time_elapsed = millis() - starttime;
31     measuring = false;
32
33     float cap = (float)time_elapsed / R; // C = t / R
34
35     Serial.print("The capacitance is: ");
36     Serial.print(cap, 6);
37     Serial.println(" nF");
38
39     Serial.print("Reached threshold at time: ");
40     Serial.print(time_elapsed);
41     Serial.println(" ms");
42   }
43 }
44
```

Errors:

- 1) ADC Resolution:** Arduino ADC resolution $\approx 4.88 \text{ mV}$ so Threshold crossing may be detected slightly early or late
 - 2) Noise:** Can be caused by Analog pin fluctuations
 - 3) Timing Resolution:** micros () resolution is $\sim 4 \mu\text{s}$ on Arduino Uno and so it limits precision for small capacitance values.
-


(TASK C)

Voltage Divider Equation:

$$V_{out} = V_{source} \times \frac{R_x}{R_{ref} + R_x}$$

Rearranging to Find Unknown Resistance:

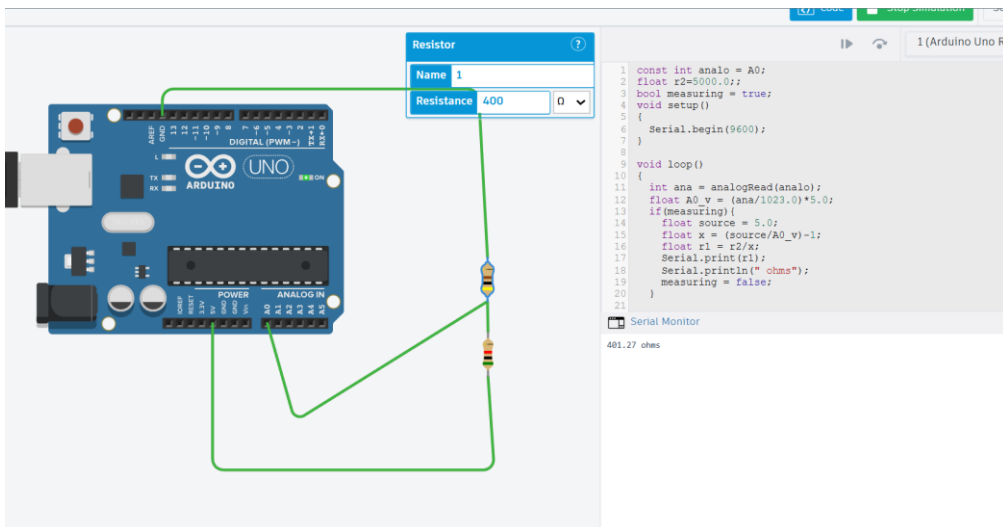
$$R_x = R_{ref} \times \frac{V_{out}}{V_{source} - V_{out}}$$



OUTPUT: Using the simple Voltage divider formula, we calculate the logic for unknown resistance. (The serial monitor gives the value of the unknown resistance).

The known resistance in this case is $5\text{k}\Omega$.

Actual Value of unknown R (in Ω)	Experimental Value of unknown R (in Ω)
400	401.27
21	19.63
45	44.38

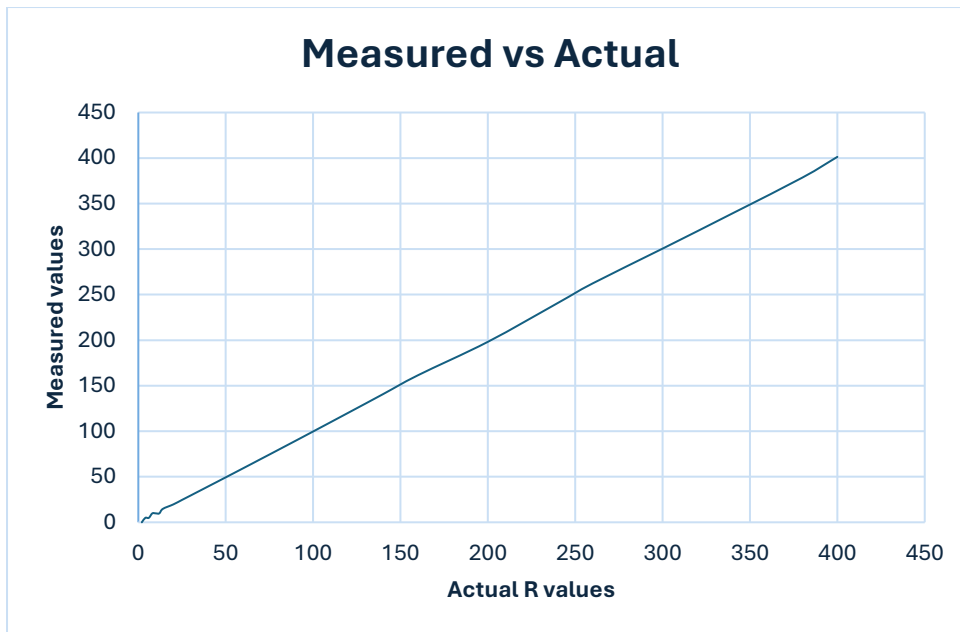

ERROR & WHY NON-IDEALITY?

In the graph, in the **mid-high range** of resistor values, the graph is approximately linear and the fluctuations that happen are most likely caused by variations in **Reference voltage which is not exactly 5.000 V**

The Arduino assumes $V_{ref} = 5.0V$ but in reality, USB power fluctuates ($\approx 4.8\text{--}5.1\text{ V}$).

In the region where R is very small, the graph is not at all linear. This is due to the following reason-

When $R_x \ll R_{ref}$: $V_{out} \approx V_{in} \frac{R_x}{R_{ref}}$. As a result, the output voltage measured is very small at the Analog pin.

These voltages correspond to very few ADC counts:

$$ADC = \frac{V_{out}}{5} \times 1023$$

Example:

- $0.05\text{ V} \approx 10\text{ counts}$
- $0.10\text{ V} \approx 20\text{ counts}$

Due to this, **even a single ADC count error can make a huge resistance error.**